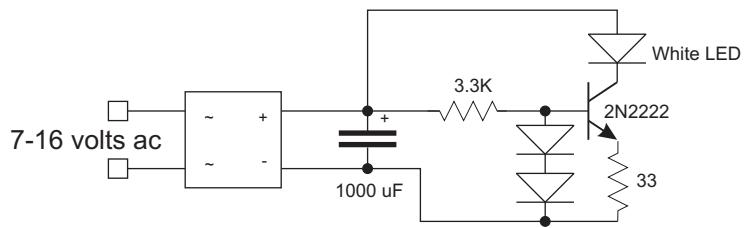


Low drop out voltage constant current source LED lighting  
Norbert Doerry  
December 2012



Current through LED  
is about .65 volts divided by 33 ohms  
which is about 20 mA. Modifying the  
resistor value will modify the LED current.